

Homework Assignment No. 2 - Solutions

Problem 1 - (10 points)

a) For the emitter follower output stage shown below, find the value of R_I for maximum efficiency and find the value of that efficiency. $V_{CC} = -V_{EE} = 2.5V$, $V_{CE(sat)} = 0.2V$, $R_L = 10k\Omega$, $V_{BE(on)} = 0.7V$.

b) The load resistance R_L is replaced with a capacitor of 100pF. If the input voltage suddenly drops from 2.5V to -2.5V, explain what happens at the output and accurately sketch the output voltage as a function of time, specifying its initial and final values and time interval.

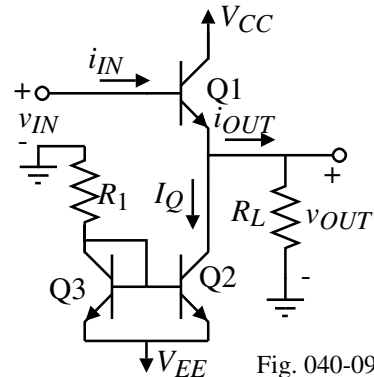


Fig. 040-09

Solution

The I_Q for maximum efficiency is found as,

$$I_Q = \left(\frac{V_{CC} - V_{CE(sat)}}{R_L} \right) = 230\mu A$$

$$R_I = \left(\frac{-V_{EE} - V_{BE}}{I_Q} \right) = 7.826k\Omega$$


$$P_{L(max)} = \left(\frac{V_{CC} - V_{CE(sat)}}{\sqrt{2}} \right) \left(\frac{I_Q}{\sqrt{2}} \right) = 0.5(2.3V)(0.23mA) = 0.2645mW$$

$$P_{supply} = 2V_{CC}I_Q = 2(2.5)(0.23mA) = 1.15mW$$

$$\eta = \frac{P_{L(max)}}{P_{supply}} = \frac{1}{4} \left(1 - \frac{V_{CE(sat)}}{V_{CC}} \right) = 23\%$$


b) The output would slew under such condition. The current will be limited by the bias current:

$$\text{Slew rate} = 0.23mA/100pF = 2.3V/\mu s$$

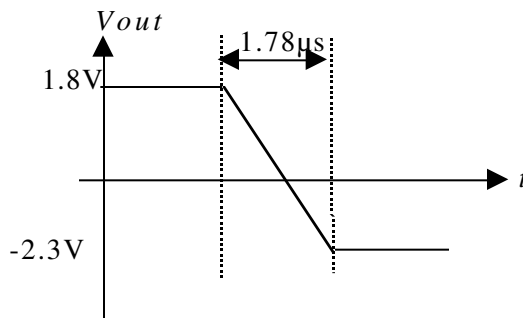

Problem 2 - (10 points)

Six versions of a source follower are shown below. Assume that $K'_N = 2K'_P$, $\lambda_P = 2\lambda_N$, all W/L ratios of all devices are equal, and that all bias currents in each device are equal. Neglect bulk effects in this problem and assume no external load resistor. Identify which circuit or circuits have the following characteristics: (a.) highest small-signal voltage gain, (b.) lowest small-signal voltage gain, (c.) the highest output resistance, (d.) the lowest output resistance, (e.) the highest $v_{out(max)}$ and (f.) the lowest $v_{out(max)}$.

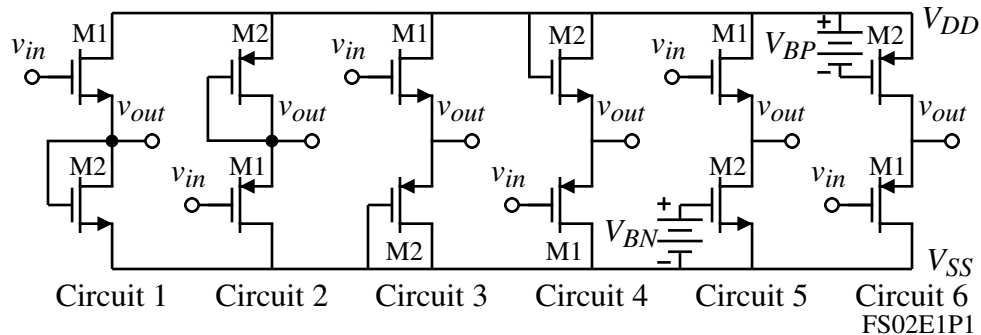Solution

(a.) and (b.) - Voltage gain.

Small signal model:

$$\text{The voltage gain is found as: } \frac{v_{out}}{v_{in}} = \frac{g_m}{g_m + G_L}$$

where G_L is the load conductance. Therefore we get:

Circuit	1	2	3	4	5	6
$\frac{v_{out}}{v_{in}}$	$\frac{g_{mN}}{g_{mN} + g_{mN}}$	$\frac{g_{mP}}{g_{mP} + g_{mP}}$	$\frac{g_{mN}}{g_{mN} + g_{mP}}$	$\frac{g_{mP}}{g_{mP} + g_{mN}}$	$\frac{g_{mN}}{g_{mN} + g_{dsN} + g_{dsP}}$	$\frac{g_{mP}}{g_{mP} + g_{dsN} + g_{dsP}}$

But $g_{mN} = \sqrt{2} g_{mP}$ and $g_{dsN} = 0.5g_{dsP}$, therefore

Circuit	1	2	3	4	5	6
$\frac{v_{out}}{v_{in}}$	$\frac{1}{2}$	$\frac{1}{2}$	0.5858	0.4142	$\frac{g_{mP}}{g_{mP} + (g_{dsP} + g_{dsN})/\sqrt{2}}$	$\frac{g_{mP}}{g_{mP} + g_{dsP} + g_{dsN}}$

Thus, circuit 5 has the highest gain and circuit 4 the lowest gain

(c.) and (d.) - Output resistance.

The denominators of the first table show the following:

Ckt.6 has the highest output resistance and Ckt. 1 the lowest output resistance.

(e.) Assuming no current has to be provided by the output, circuits 2, 4, and 6 can pull the output to V_{DD} . \therefore Circuits 2, 4 and 6 have the highest output swing.

(f.) Assuming no current has to be provided by the output, circuits 1, 3, and 5 can pull the output to ground. \therefore Circuits 1, 3 and 5 have lowest output swing.

Summary

(a.) Ckt. 5 has the highest voltage gain

(d.) Ckt. 1 has the lowest output resistance

(b.) Ckt. 4 has the lowest voltage gain


(e.) Ckts. 2,4 and 6 have the highest output

(c.) Ckt. 6 has the highest output resistance

(f.) Ckts. 1,3 and 5 have the lowest output

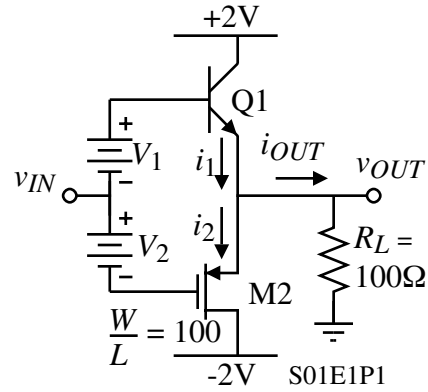Problem 3 - (10 points)

A push-pull follower is shown which uses an NPN BJT and a p-channel MOSFET. In this problem, ignore the bulk effect, the channel length modulation, and the Early voltage. The parameters for the NPN BJT are $\beta_F = 100$, $I_s = 10\text{fA}$ and $V_t = 25.9\text{mV}$. The model parameters for the PMOS are $K_P' = 50\mu\text{A}/\text{V}^2$ and $V_T = -0.7\text{V}$. (a.) Find the value of the dc batteries, V_1 and V_2 , which will cause $100\mu\text{A}$ to flow in Q_1 and M_2 when the dc value of $v_{IN} = 0\text{VDC}$. (b.) Find the small-signal input resistance, output resistance and voltage gain when the dc value of $v_{IN} = 0\text{VDC}$.



Solution


(a.) $V_1 = V_{BE1} = V_t \ln\left(\frac{i_C}{I_s}\right) = 0.0259 \ln\left(\frac{100\mu\text{A}}{10\text{fA}}\right) = 0.5964\text{V}$ $V_1 = 0.5964\text{V}$

$V_2 = V_{SG2} = \sqrt{\frac{2I_D}{K_P'(W/L)}} + |V_{TP}| = \sqrt{\frac{2 \cdot 100}{50 \cdot 100}} + 0.7 = 0.9\text{V}$ $V_2 = 0.9\text{V}$

(b.) Small-signal model (simplified):

$g_{m1} = \frac{I_{C1}}{V_t} = \frac{100\mu\text{A}}{25.9\text{mV}} = 3.86\text{mS}$

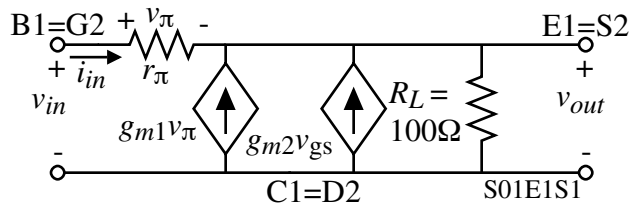$r_{\pi 1} = \frac{1 + \beta_F}{g_{m1}} = 26.159\text{k}\Omega$



$g_{m2} = \sqrt{\frac{2K_P'W_2I_{D2}}{L_2}} = \sqrt{2 \cdot 50 \cdot 100 \cdot 100} = 1\text{mS}$

$R_{in} : v_{in} = r_{\pi 1} i_{in} + (i_{in} + g_{m1} v_{\pi} + g_{m2} v_{gs2}) R_L = r_{\pi 1} i_{in} + (i_{in} + g_{m1} r_{\pi 1} i_{in} + g_{m2} r_{\pi 1} i_{in}) R_L$

$R_{in} = \frac{v_{in}}{i_{in}} = r_{\pi 1} + R_L + g_{m1} r_{\pi 1} R_L + g_{m2} r_{\pi 1} R_L = r_{\pi 1} + R_L(1 + \beta_F) + g_{m2} r_{\pi 1} R_L$

$\therefore R_{in} = 26.159\text{k}\Omega + 101 \cdot 100\Omega + 1 \cdot 26.159\text{k}\Omega \cdot 0.1 = 38.875\text{k}\Omega$ $R_{in} = 38.875\text{k}\Omega$

$R_{out} : R_{out} = \frac{1}{g_{m1}} \parallel \frac{1}{g_{m2}} = \frac{1}{3.86\text{mS} + 1\text{mS}} = 205.8\text{k}\Omega$ $R_{out} = 205.8\text{k}\Omega$

$\frac{v_{out}}{v_{in}} : \frac{v_{out}}{v_{in}} = \frac{v_{out}}{i_{in}} \frac{i_{in}}{v_{in}} = \frac{R_L(1 + \beta_F) + g_{m2} r_{\pi 1} R_L}{r_{\pi 1} + R_L(1 + \beta_F) + g_{m2} r_{\pi 1} R_L} = \frac{12.716}{38.875} = 0.3271$

$\frac{v_{out}}{v_{in}} = 0.3271\text{V/V}$

Problem 4 - (10 points)

Find an algebraic expression for the voltage gain, v_{out}/v_{in} , and the output resistance, R_{out} , of the source follower shown in terms of the small-signal model parameters, g_m and R_L (ignore r_{ds}). If the bias current is 1mA find the numerical value of the voltage gain and the output resistance. Assume that $K_N' = 110\mu\text{A}/\text{V}^2$, $V_{TN} = 0.7\text{V}$, and $K_P' = 50\mu\text{A}/\text{V}^2$, $V_{TP} = -0.7\text{V}$.

Solution

A small-signal model for this circuit is shown below neglecting r_{ds} of the transistors.

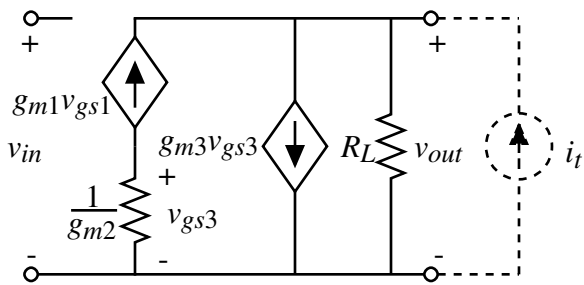


Fig. S03E1S1

$$g_{m1}(v_{out} - v_{in}) \left(1 + \frac{g_{m3}}{g_{m2}} \right) = G_L v_{out}$$

$$\therefore \frac{v_{out}}{v_{in}} = \frac{g_{m1} \left(1 + \frac{g_{m3}}{g_{m2}} \right)}{g_{m1} \left(1 + \frac{g_{m3}}{g_{m2}} \right) + G_L}$$

Setting $v_{in} = 0$ and applying i_t and solving for v_{out} and ignoring R_L gives,

$$i_t = g_{m3}v_{gs3} + g_{m1}v_{out} = g_{m3} \left(\frac{g_{m1}}{g_{m2}} \right) v_{out} + g_{m1}v_{out}$$

$$\therefore \frac{v_{out}}{i_t} = R_{out} = \frac{1}{g_{m1} \left(1 + \frac{g_{m3}}{g_{m2}} \right)}$$


Note that the 1mA splits between M1(M2) and M3 in a ratio of 1 to 100. Therefore, $I_{D1} = I_{D2} = 9.9\mu\text{A}$ and $I_{D3} = 990.1\mu\text{A}$.

$$\therefore g_{m1} = \sqrt{2 \cdot 110 \cdot 100 \cdot 9.9} = 466.71\mu\text{S}, \quad g_{m2} = \sqrt{2 \cdot 50 \cdot 1 \cdot 9.9} = 31.47\mu\text{S}$$

$$\text{and } g_{m3} = \sqrt{2 \cdot 110 \cdot 100 \cdot 990.1} = 3146.7\mu\text{S}$$

$$\frac{v_{out}}{v_{in}} = \frac{466.71 \cdot 101}{466.71 \cdot 101 + 1/50} = \frac{47.137}{47.137 + 20} = \underline{\underline{0.702 \text{ V/V}}}$$
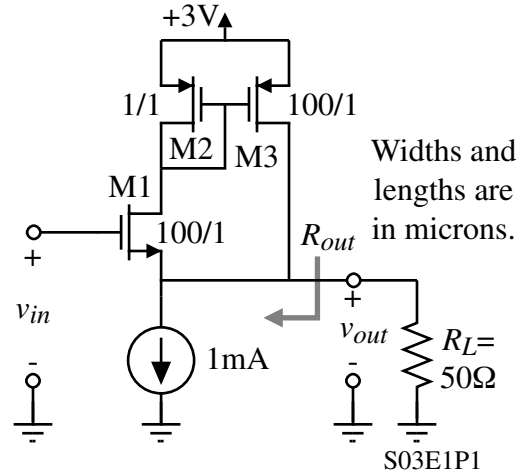
$$R_{out} = \frac{1000}{47.137} = \underline{\underline{21.2\Omega}}$$



Summing currents at the output node gives,


$$g_{m1}v_{gs1} = g_{m3}v_{gs3} + G_L v_{out}$$

$$\text{Also, } v_{gs3} = -g_{m1}v_{gs1}(1/g_{m2})$$


$$\therefore g_{m1}v_{gs1} = g_{m3} \left(-\frac{g_{m1}}{g_{m2}} \right) v_{gs1} + G_L v_{out}$$

$$g_{m1}v_{gs1} \left(1 + \frac{g_{m3}}{g_{m2}} \right) = G_L v_{out} \rightarrow$$

Problem 5 - Design Prob. #1

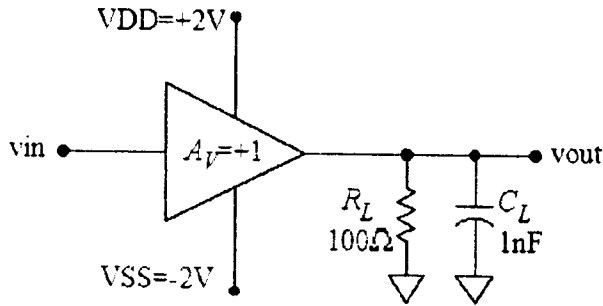

Output swing	-1.25V - 1.06V
SR	> 10V/usec
DC gain	= 1
efficiency	= 30.6%
score	40

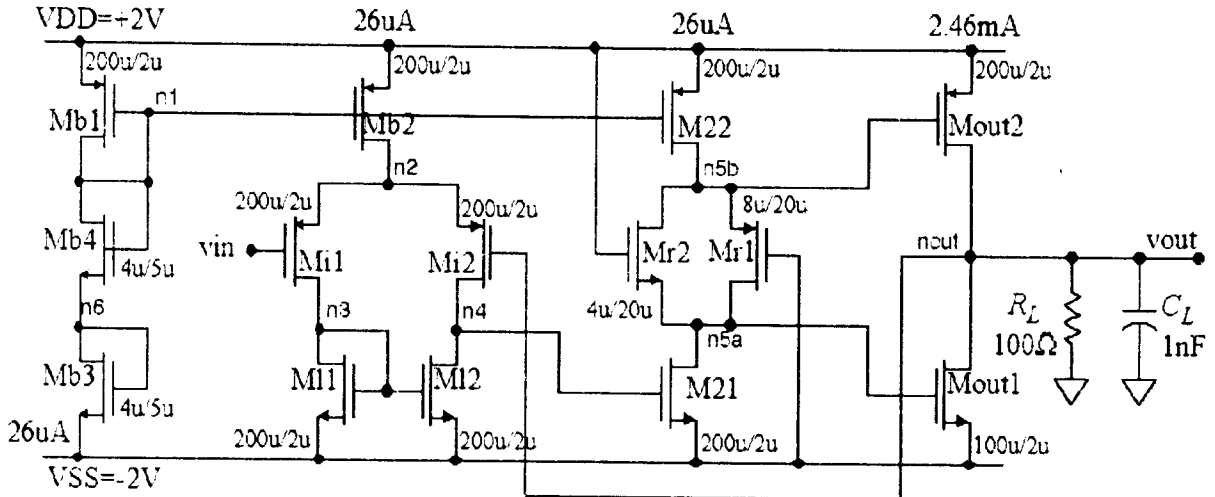


A three stage amplifier connected in unity gain configuration is used as the output buffer. The first two stages are class-A whereas the last stage is class-AB.

1nF load capacitance makes the pole present at node nout the dominant pole. Therefore, there is no need to apply additional compensation to the three stage amplifier.

DC gain of the amplifier in unity gain configuration = $A_v / (1 + A_v)$
 where $A_v \propto g_m^3 r_{ds}^3$

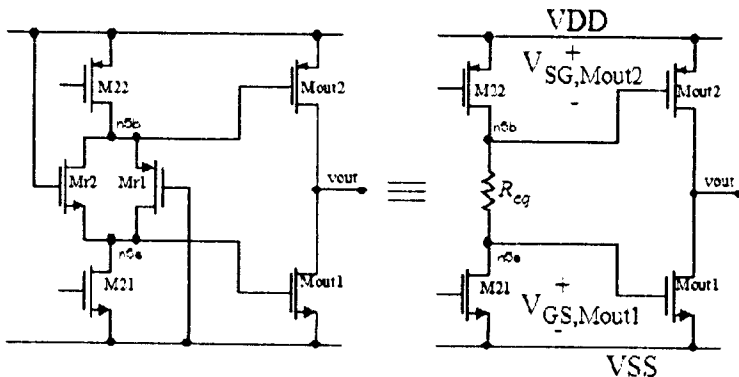Output impedance of the unity gain buffer = $r_{ds} / (1 + A_v)$.



$$VDD - VSS = V_{GS,Mout1} + V_{SG,Mout2} + I_{d,M21} R_{eq}$$

$I_{d,M21}$: quiescent drain current of M21.

Mr1 and Mr2 act as a linear resistor, allowing a voltage drop between n5a and n5b. The net result is reduced quiescent current at the output stage.

```

*output buffer
.option brief
.options
+ post
+ ingold=2
+ scale=1e-6
+ accurate
+ delmax=0.5n
+ method=gear lvltim=2
+ probe
*

vdd dd 0 dc 2v
vss ss 0 dc -2v
*vin in 0 dc 0v
vin in 0 sin (0 1.5 100k 0)
*vin in 0 pulse (-1 1 2u 2n 2n 1u 2u)

mb1 n1 n1 dd dd cmosp l=2u w=200u
mb2 n2 n1 dd dd cmosp l=2u w=200u
mb3 n6 n6 ss ss cmosn l=5u w=4u
mb4 n1 n1 n6 ss cmosn l=5u w=4u
mi1 n3 in n2 n2 cmosp l=2u w=200u
mi2 n4 nout n2 n2 cmosp l=2u w=200u
ml1 n3 n3 ss ss cmosn l=2u w=200u
ml2 n4 n3 ss ss cmosn l=2u w=200u
m21 n5a n4 ss ss cmosn l=2u w=200u
m22 n5b n1 dd dd cmosp l=2u w=200u
mr1 n5a ss n5b dd cmosp l=20u w=8u
mr2 n5b dd n5a ss cmosn l=20u w=4u
mout1 nout n5a ss ss cmosn l=2u w=100u
mout2 nout n5b dd dd cmosp l=2u w=200u
r1 nout 0 100
cl nout ss 1nF
*.dc vin -2 2 1m
.meas tran current_vdd avg i(vdd) from=0 to=50u
.meas tran power_vdd param='4*current_vdd'

.tran 1u 50u
.model cmosn nmos kp=110u vto=0.7 lambda=0.01 gamma=0.4 phi=0.7
.model cmosp pmos kp=50u vto=-0.7 lambda=0.01 gamma=0.7 phi=0.8
.probe v(in) v(n1) v(n2) v(n3) v(n4) v(n5) v(nout) v(n5a) v(n5b) i(vdd) i(vss)
.op
.end

```

calculates the average current drawn from VDD and power

***** operating point information tnom= 25.000 temp= 25.000

***** operating point status is all simulation time is 0.
node =voltage node =voltage node =voltage

+0:dd	= 2.000e+00	0:in	= 0.	0:n1	= 1.197e+00
+0:n2	= 7.723e-01	0:n3	=-1.250e+00	0:n4	=-1.230e+00
+0:n5a	=-3.641e-01	0:n5b	= 3.185e-01	0:n6	=-5.283e-01
+0:nout	=-1.441e-05	0:ss	=-2.000e+00		

**** voltage sources

subckt			
element	0:vdd	0:vss	0:vin
volts	2.000e+00	-2.000e+00	0.
current	-2.537e-03	2.537e-03	0.
power	5.073e-03	5.074e-03	0.

total voltage source power dissipation= 1.015e-02 watts

**** resistors

subckt	
element	0:r1
r value	1.000e+02
v drop	-1.441e-05
current	-1.441e-07
power	2.075e-12

**** mosfets

subckt						
element	0:mb1	0:mb2	0:mb3	0:mb4	0:mi1	0:mi2
model	0:cmosp	0:cmosp	0:cmosn	0:cmosn	0:cmosp	0:cmosp
id	-2.659e-05	-2.670e-05	2.659e-05	2.659e-05	-1.335e-05	-1.335e-05
ibs	0.	0.	0.	-1.472e-14	0.	0.
ibd	8.027e-15	1.228e-14	-1.472e-14	-3.197e-14	2.023e-14	2.003e-14
vgs	-8.027e-01	-8.027e-01	1.471e+00	1.725e+00	-7.723e-01	-7.724e-01
vds	-8.027e-01	-1.227e+00	1.471e+00	1.725e+00	-2.023e+00	-2.003e+00
vbs	0.	0.	0.	-1.471e+00	0.	0.
vth	-7.000e-01	-7.000e-01	7.000e-01	9.548e-01	-7.000e-01	-7.000e-01
vdsat	-1.027e-01	-1.027e-01	7.717e-01	7.708e-01	-7.235e-02	-7.236e-02
beta	5.040e-03	5.061e-03	8.930e-05	8.952e-05	5.101e-03	5.100e-03
gam eff	7.000e-01	7.000e-01	4.000e-01	4.000e-01	7.000e-01	7.000e-01
gm	5.177e-04	5.199e-04	6.891e-05	6.900e-05	3.690e-04	3.690e-04
gds	2.638e-07	2.638e-07	2.620e-07	2.614e-07	1.308e-07	1.309e-07
gmb	2.026e-04	2.034e-04	1.647e-05	9.364e-06	1.444e-04	1.444e-04
cdtot	1.478e-28	2.261e-28	0.	0.	3.726e-28	3.689e-28
cgtot	9.856e-26	9.864e-26	4.651e-27	4.641e-27	1.009e-25	1.009e-25
cstot	9.208e-26	9.208e-26	4.604e-27	4.604e-27	9.208e-26	9.208e-26
cbtot	6.331e-27	6.331e-27	0.	0.	8.414e-27	8.412e-27
cgs	9.208e-26	9.208e-26	4.604e-27	4.604e-27	9.208e-26	9.208e-26
cgd	1.478e-28	2.261e-28	0.	0.	3.726e-28	3.689e-28

subckt						
element	0:m11	0:m12	0:m21	0:m22	0:mr1	0:mr2
model	0:cmosn	0:cmosn	0:cmosn	0:cmosp	0:cmosp	0:cmosn
id	1.335e-05	1.335e-05	2.682e-05	-2.682e-05	1.100e-05	1.582e-05
ibs	0.	0.	0.	0.	2.364e-14	-1.636e-14
ibd	-7.491e-15	-7.693e-15	-1.636e-14	1.682e-14	1.682e-14	-2.318e-14

vgs	7.491e-01	7.491e-01	7.693e-01	-8.027e-01	-1.635e+00	2.364e+00
vds	7.491e-01	7.693e-01	1.635e+00	-1.681e+00	6.826e-01	6.826e-01
vbs	0.	0.	0.	0.	2.364e+00	-1.635e+00
vth	7.000e-01	7.000e-01	7.000e-01	-7.000e-01	-1.176e+00	9.767e-01
vdsat	4.908e-02	4.908e-02	6.927e-02	-1.027e-01	-6.826e-01	6.826e-01
beta	1.108e-02	1.108e-02	1.118e-02	5.084e-03	2.014e-05	2.215e-05
gam eff	4.000e-01	4.000e-01	4.000e-01	7.000e-01	7.000e-01	4.000e-01
gm	5.440e-04	5.441e-04	7.744e-04	5.222e-04	1.375e-05	1.512e-05
gds	1.325e-07	1.325e-07	2.639e-07	2.638e-07	9.357e-06	1.577e-05
gmb	1.300e-04	1.301e-04	1.851e-04	2.044e-04	3.054e-06	1.979e-06
cdtot	1.380e-28	1.417e-28	3.013e-28	3.097e-28	3.380e-26	1.032e-26
cgtot	9.994e-26	9.994e-26	9.836e-26	9.873e-26	5.208e-26	2.669e-26
cstot	9.208e-26	9.208e-26	9.208e-26	9.208e-26	1.810e-26	1.633e-26
cbtot	7.715e-27	7.715e-27	5.970e-27	6.331e-27	1.729e-28	0.
cgs	9.208e-26	9.208e-26	9.208e-26	9.208e-26	1.810e-26	1.633e-26
cgd	1.380e-28	1.417e-28	3.013e-28	3.097e-28	3.380e-26	1.032e-26

```

subckt
element 0:mout1 0:mout2
model 0:cmosn 0:cmosp
id 2.457e-03 -2.457e-03
ibs 0. 0.
ibd -2.000e-14 2.000e-14
vgs 1.635e+00 -1.681e+00
vds 2.000e+00 -2.000e+00
vbs 0. 0.
vth 7.000e-01 -7.000e-01
vdsat 9.359e-01 -9.815e-01
beta 5.610e-03 5.100e-03
gam eff 4.000e-01 7.000e-01
gm 5.250e-03 5.006e-03
gds 2.409e-05 2.408e-05
gmb 1.255e-03 1.959e-03
cdtot 1.842e-28 3.683e-28
cgtot 4.651e-26 9.323e-26
cstot 4.604e-26 9.208e-26
cbtot 2.788e-28 7.758e-28
cgs 4.604e-26 9.208e-26
cgd 1.842e-28 3.683e-28

```

Opening plot unit= 15
file=./buffer.tr0

```

*****
*current source
***** transient analysis tnom= 25.000 temp= 25.000
*****
current_vdd = -4.5829E-03 from= .0000E+00 to= 5.0000E-05
power_vdd = -1.8332E-02

```

average power dissipation

***** job concluded

```

***** Star-HSPICE -- 97.2.1 (970915) 14:15:30 98/06/01 pa
*****

```

```

*current source
***** job statistics summary tnom= 25.000 temp= 25.000
*****

```

total memory used 159 kbytes

nodes = 12 # elements= 19



diodes= 0 # bjts = 0 # jfets = 0 # mosfets = 14

analysis	time	# points	tot. iter	conv.iter
op point	.11	1	7	
transient	214.78	51	200387	100051 rev= 27
readin	.10			
errchk	.08			
setup	.00			
output	1.55			


total cpu time 216.72 seconds
job started at 14:15:30 98/06/01
job ended at 14:19:15 98/06/01

lic: Release token(s)
HSPICE job buffer.sp completed.
Mon Jun 1 14:19:15 PDT 1998

OUTPUT BUFFER

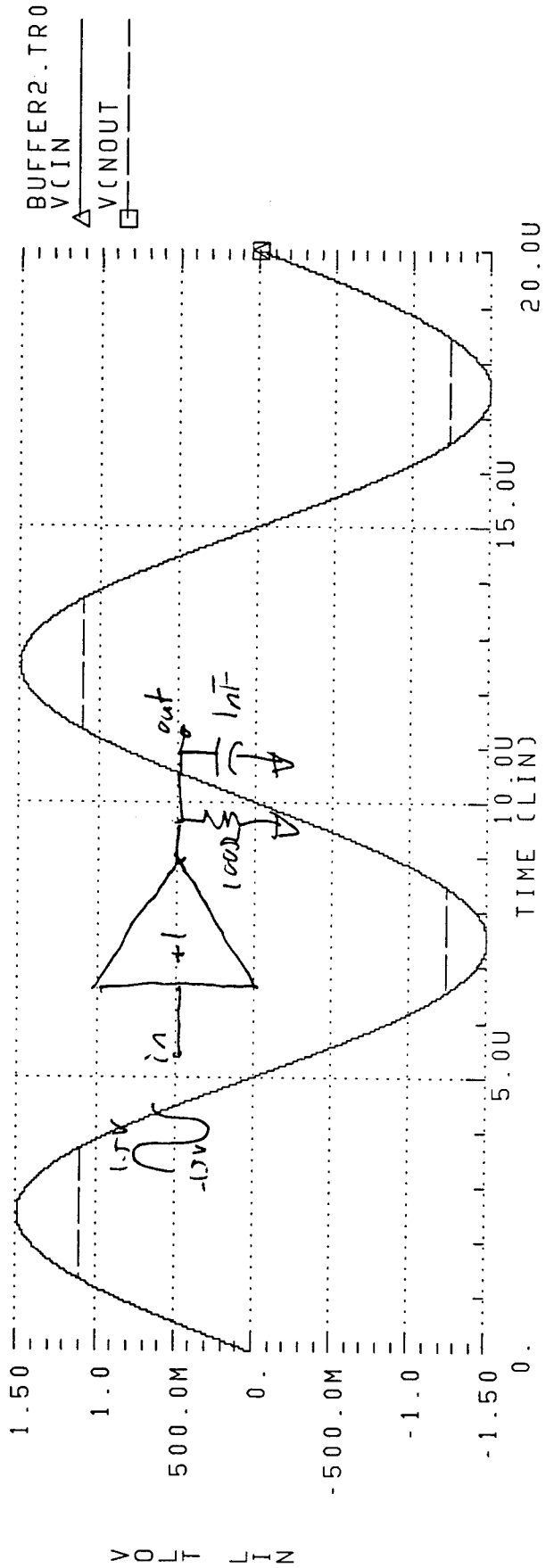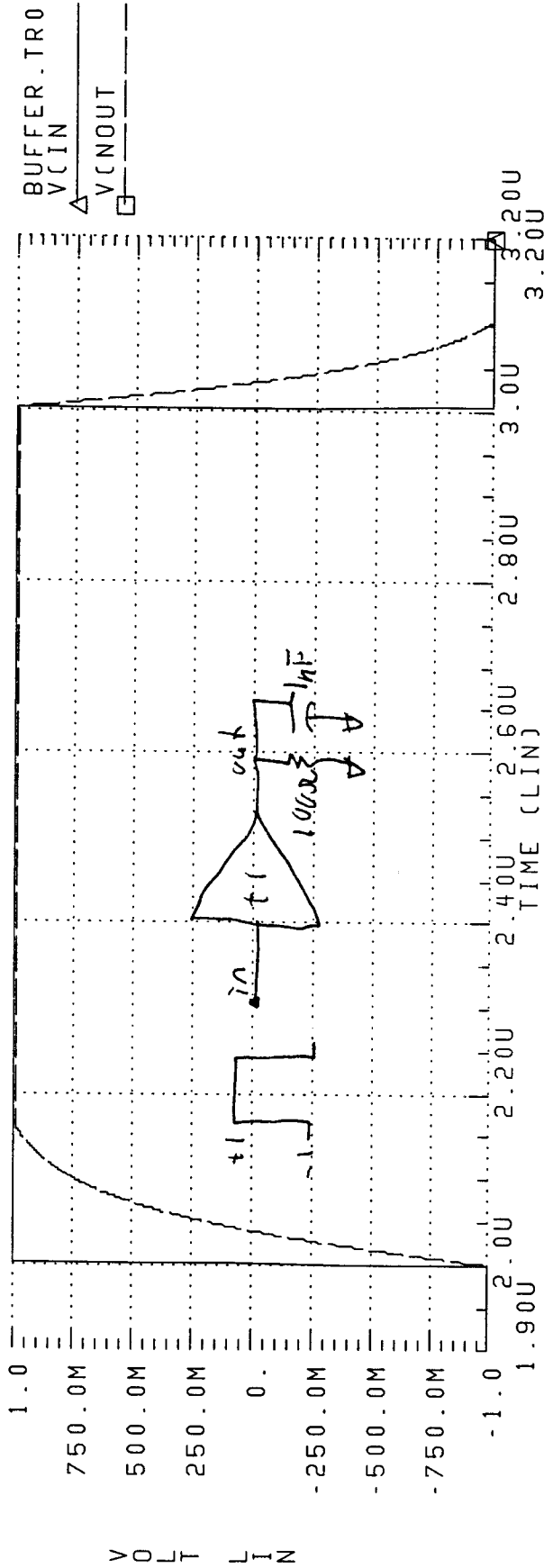

OUTPUT BUFFER

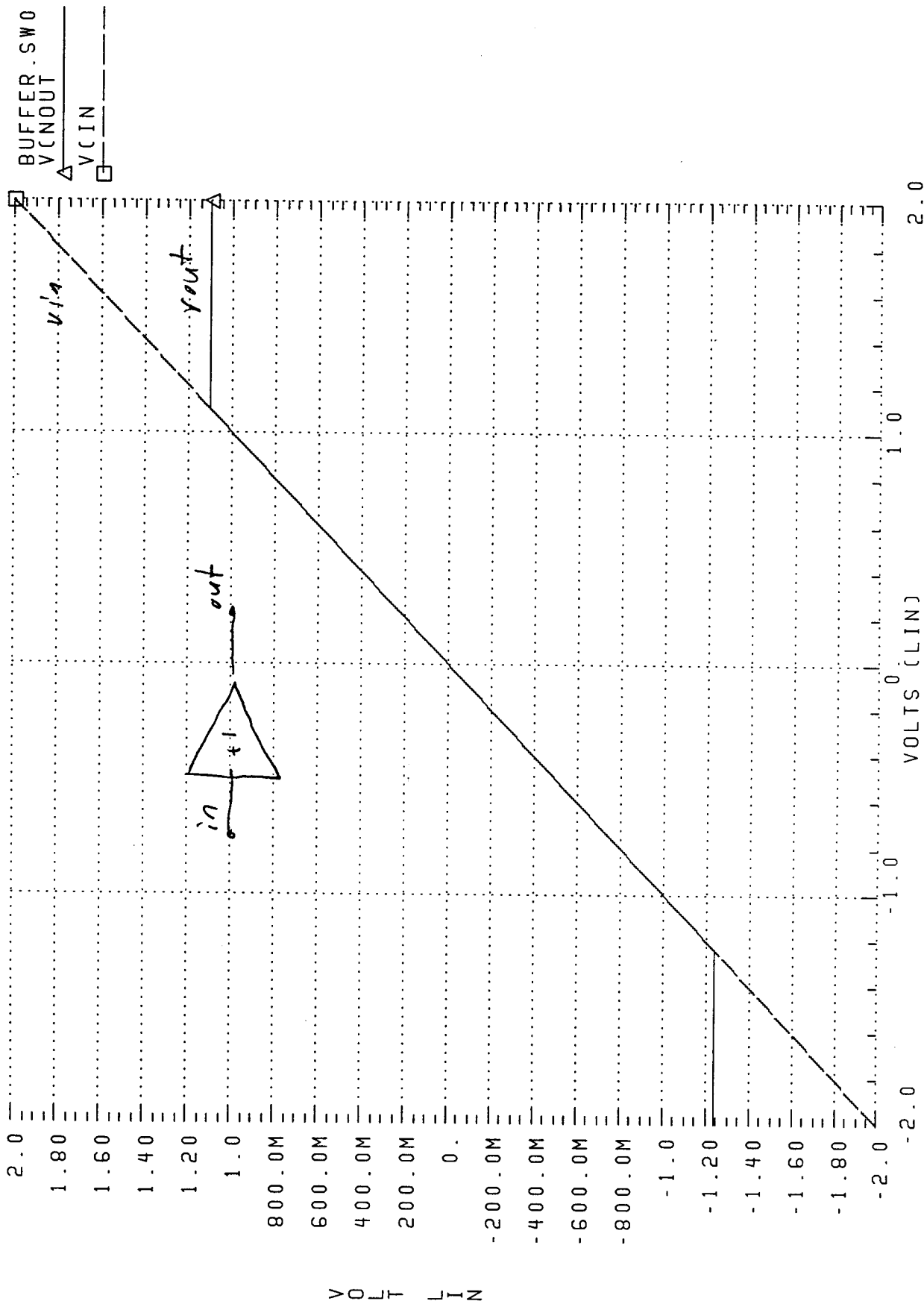

BUFFER.SW0
VCNOUT
VCIN

