

Homework Assignment No. 12

Problem 1 - (10 points)

Find the GB of a two-stage op amp using Miller compensation using a nulling resistor that has 60° phase margin where the second pole is -10×10^6 rads/sec and two higher poles both at -100×10^6 rads/sec. Assume that the RHP zero is used to cancel the second pole and that the load capacitance stays constant. If the input transconductance is $500 \mu\text{A/V}$, what is the value of C_c ?

Solution

The resulting higher-order poles are two at -100×10^6 radians/sec. The resulting phase margin expression is,

$$\text{PM} = 180^\circ - \tan^{-1}(A_v(0)) - 2 \tan^{-1}\left(\frac{GB}{10^7}\right) = 90^\circ - 2 \tan^{-1}\left(\frac{GB}{10^7}\right) = 60^\circ$$

$$\therefore 30^\circ = 2 \tan^{-1}\left(\frac{GB}{10^7}\right) \rightarrow \left(\frac{GB}{10^7}\right) = \tan(15^\circ) = 0.2679$$

$$GB = 2.679 \times 10^7 = \frac{g_{m1}}{C_c} \rightarrow C_c = \frac{500 \times 10^{-6}}{26.79 \times 10^7} = \underline{\underline{18.66 \text{ pF}}}$$

Problem 2 – P7.2-4

Use the technique of Ex. 7.2-2 to extend the GB of the cascode op amp of Ex. 6.5-2 as much as possible that will maintain 60° phase margin. What is the minimum value of C_L for the maximum GB ?

Solution

Assuming all channel lengths to be $1 \mu\text{m}$, the total capacitance at the source of M7 is

$$C_7 = C_{gs7} + C_{bd7} + C_{gd6} + C_{bd6}$$

$$\text{or, } C_7 = 75 + 51 + 9 + 51 = 186 \text{ fF}$$

$$g_{m7} = 707 \mu\text{S}$$

Thus, the pole at the source of M7 is

$$p_{S7} = -\frac{g_{m7}}{C_7} = -605 \text{ MHz.}$$

The total capacitance at the source of M12 is

$$C_{12} = C_{gs12} + C_{bd12} + C_{gd11} + C_{bd11}$$

$$\text{or, } C_{12} = 34 + 29 + 4 + 29 = 96 \text{ fF}$$

$$g_{m12} = 707 \mu\text{S}$$

Thus, the pole at the source of M12 is

$$p_{S12} = -\frac{g_{m12}}{C_{12}} = -1170 \text{ MHz.}$$

The total capacitance at the drain of M4 is

$$C_4 = C_{gs4} + C_{gs6} + C_{bd4} + C_{gd2} + C_{bd2}$$

$$\text{or, } C_4 = 43 + 75 + 21 + 3 + 19 = 161 \text{ fF}$$

$$g_{m4} = 283 \mu\text{S}$$

Problem 2 - Continued

Thus, the pole at the drain of M4 is

$$p_{D4} = -\frac{g_{m4}}{C_4} = -280 \text{ MHz.}$$

The total capacitance at the drain of M8 is

$$C_8 = C_{gd8} + C_{bd8} + C_{gs10} + C_{gs12}$$

or, $C_8 = 9 + 51 + 34 + 34 = 128 \text{ fF}$

$$R_2 + \frac{1}{g_{m10}} = 3.4 \text{ K}\Omega$$

Thus, the pole at the drain of M8 is

$$p_{D8} = -\frac{1}{\left(R_2 + \frac{1}{g_{m10}}\right)C_8} = -366 \text{ MHz.}$$

For a phase margin of 60° , we have

$$PM = 180^\circ - \left[90^\circ - \left\{ \tan^{-1}\left(\frac{GB}{p_{S7}}\right) + \tan^{-1}\left(\frac{GB}{p_{S12}}\right) + \tan^{-1}\left(\frac{GB}{p_{D4}}\right) + \tan^{-1}\left(\frac{GB}{p_{D8}}\right) \right\} \right]$$

Solving the above equation

$$GB \cong 65 \text{ MHz.}$$

And, $A_v = 6925 \text{ V/V}$

Thus, $p_1 = 9.39 \text{ KHz}$, and $C_L \geq 1.54 \text{ pF}$

Problem 3 - Problem 7.3-1

Compare the differential output op amps of Fig. 7.3-3, 7.3-5, 7.3-6, 7.3-7, 7.3-8 and 7.3-10 from the viewpoint of (a.) noise, (b.) $PSRR$, (c.) $ICMR$ [$V_{ic}(\text{max})$ and $V_{ic}(\text{min})$], (d.) $OCMR$ [$V_o(\text{max})$ and $V_o(\text{min})$], (e.) SR assuming all input differential currents are identical, and (f.) power dissipation if all current of the input differential amplifiers are identical and power supplies are equal.

Solution

	Fig. 7.3-3	Fig. 7.3-5	Fig. 7.3-6	Fig. 7.3-7	Fig. 7.3-8	Fig. 7.3-10
Noise	Good	Poor	Good	Poor	Okay	Poor
$PSRR$	Poor	Good	Poor	Good	Good	Good
$ICMR$						
$V_{ic}(\text{max})$	$V_{DD}-V_{ON}$	$V_{DD}+V_T$	$V_{DD}-V_{ON}$	$V_{DD}+V_T$	$V_{DD}-V_{ON}$	$V_{DD}-V_{ON}$
$V_{ic}(\text{min})$	$V_{SS}+$	$V_{SS}+$	$V_{SS}+$	$V_{SS}+$	$V_{SS}+$	$V_{SS}+$
	$2V_{ON}+V_T$	$2V_{ON}+V_T$	$2V_{ON}+V_T$	$2V_{ON}+V_T$	$2V_{ON}+V_T$	$3V_{ON}+2V_T$
$OCMR$						
$V_o(\text{max})$	$V_{DD}-V_{ON}$	$V_{DD}-2V_{ON}$	$V_{DD}-V_{ON}$	$V_{DD}-V_{ON}$	$V_{DD}-2V_{ON}$	$V_{DD}-2V_{ON}$
$V_o(\text{min})$	$V_{SS}+V_{ON}$	$V_{SS}+2V_{ON}$	$V_{SS}+V_{ON}$	$V_{SS}+V_{ON}$	$V_{SS}+2V_{ON}$	$V_{SS}+2V_{ON}$
SR	I_{SS}/C_c	I_{SS}/C_L	I_{SS}/C_c	I_{SS}/C_L	I_{SS}/C_L	I_{SS}/C_L

Problem 4 - Problem 7.3-7

(a.) If all transistors in Fig. 7.3-12 have a dc current of $50\mu\text{A}$ and a W/L of $10\mu\text{m}/1\mu\text{m}$, find the gain of the common mode feedback loop. (b.) If the output of this amplifier is cascoded, then repeat part (a.).

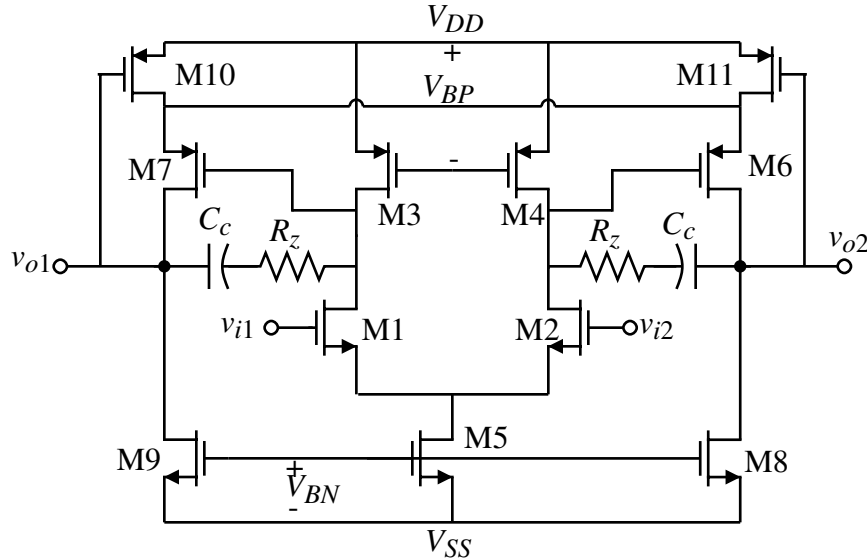
Solution

Figure 7.3-12 Two-stage, Miller, differential-in, differential-out op amp with common-mode stabilization.

The loop gain of the common-mode feedback loop is,

$$\text{CMFB Loop gain} \approx -\frac{g_{m10}}{g_{ds9}} = -g_{m10}r_{ds9} \quad \text{or} \quad -\frac{g_{m11}}{g_{ds8}} = -g_{m11}r_{ds8}$$

With $I_D = 50\mu\text{A}$ and $W/L = 10\mu\text{m}/1\mu\text{m}$, $g_{m10} = \sqrt{\frac{2K_P'WI_D}{L}} = \sqrt{2 \cdot 50 \cdot 10 \cdot 50} = 223.6\mu\text{S}$,

$$r_{dsN} = \frac{1}{\lambda_N I_D} = \frac{25}{50\mu\text{A}} = 0.5\text{M}\Omega \quad \text{and} \quad r_{dsP} = \frac{1}{\lambda_P I_D} = \frac{20}{50\mu\text{A}} = 0.4\text{M}\Omega$$

$$\therefore \boxed{\text{CMFB Loop gain} \approx -g_{m10}r_{ds9} = -223.6(0.5) = -111.8\text{V/V}}$$

If the output is cascoded, the gain becomes,

$$\begin{aligned} \text{CMFB Loop gain with cascoding} &\approx -\frac{g_{m10}}{g_{ds9}} g_m(\text{cascode})r_{ds}(\text{cascode}) \\ &= -g_{m10}\{[r_{ds9} g_m(\text{cascode})r_{ds}(\text{cascode})]\| [g_{m7}r_{ds7} (r_{ds10}\|r_{ds10})]\} \end{aligned}$$

$$g_{mP} = \sqrt{\frac{2K_N'WI_D}{L}} = \sqrt{2 \cdot 110 \cdot 10 \cdot 50} = 331.67\mu\text{S}$$

$$= -(223.6)[(0.5 \cdot 331.67 \cdot 0.5)\| (223.6)(0.4)(0.2)] = 223.6(14.7) = -3,290 \text{ V/V}$$

$$\therefore \boxed{\text{CMFB Loop gain with cascoding} \approx -3.290\text{V/V}}$$

Problem 5 – Problem 7.4-1

Calculate the gain, GB , SR and P_{diss} for the folded cascode op amp of Fig. 6.5-7b if $V_{DD} = -V_{SS} = 1.5V$, the current in the differential amplifier pair is $50nA$ each and the current in the sources, M4 and M5, is $150nA$. Assume the transistors are all $10\mu m/1\mu m$, the load capacitor is $2pF$ and that n_1 is 2.5 for NMOS and 1.5 for PMOS.

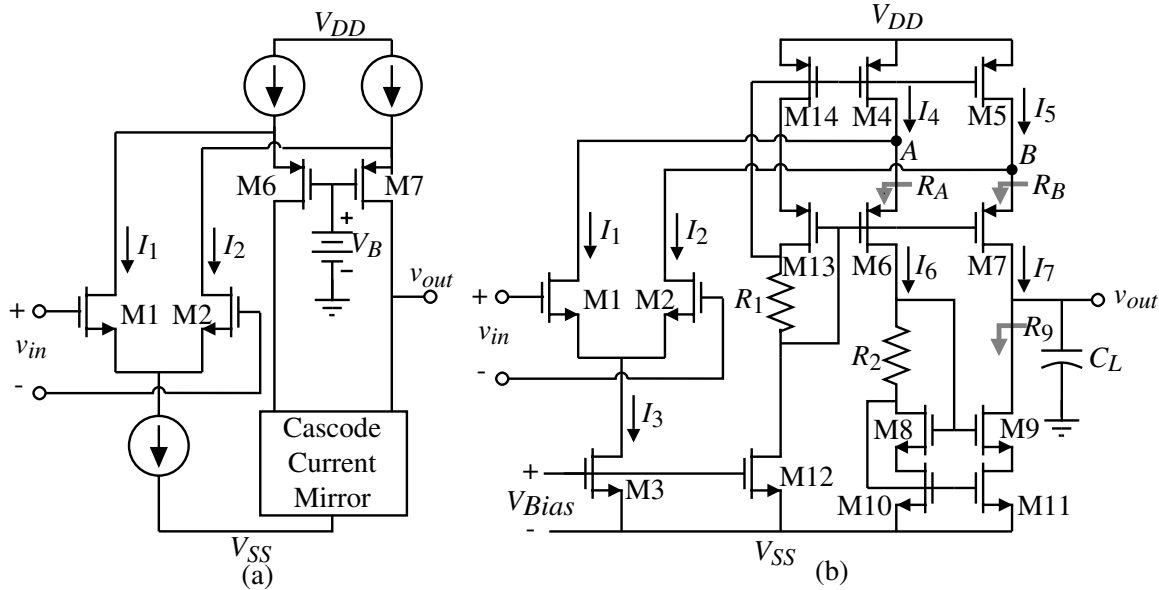


Figure 6.5-7 (a) Simplified version of an N-channel input, folded cascode op amp.
(b) Practical version (a).

Solution

$$g_{m1} = g_{m2} = \frac{I_D}{n_1(kT/q)} = \frac{50nA}{2.5 \cdot 25.9mV} = 0.772\mu S \quad \text{and} \quad r_{ds1} = r_{ds2} = \frac{1}{I_D \lambda_N} = 500M\Omega$$

$$g_{m4} = g_{m5} = \frac{I_D}{n_1(kT/q)} = \frac{150nA}{1.5 \cdot 25.9mV} = 3.861\mu S \quad \text{and} \quad r_{ds4} = r_{ds5} = \frac{1}{I_D \lambda_N} = 133M\Omega$$

$$g_{m6} = g_{m7} = \frac{I_D}{n_1(kT/q)} = \frac{100nA}{1.5 \cdot 25.9mV} = 2.574\mu S \quad \text{and} \quad r_{ds6} = r_{ds7} = \frac{1}{I_D \lambda_N} = 200M\Omega$$

$$g_{m8} = g_{m9} = g_{m10} = g_{m11} = \frac{I_D}{n_1(kT/q)} = \frac{100nA}{2.5 \cdot 25.9mV} = 1.544\mu S$$

$$\text{and } r_{ds8} = r_{ds9} = r_{ds10} = r_{ds11} = \frac{1}{I_D \lambda_N} = 250M\Omega$$

$$\text{Gain: } A_v(0) = g_{m1} R_{out}$$

$$R_{out} \approx r_{ds11} g_{m9} r_{ds9} \parallel [g_{m7} r_{ds7} (r_{ds5} \parallel r_{ds2})] = 96.5G\Omega \parallel 34.23G\Omega = 25.269G\Omega$$

$$\therefore A_v(0) = 0.772\mu S \cdot 25.269G\Omega = \underline{\underline{19,508 \text{ V/V}}}$$

$$GB = g_{m1}/C_L = 386krads/sec = \underline{\underline{61.43kHz}} \quad (\text{this assumes all other poles are greater than}$$

$$GB \text{ which is the case if } C_L \text{ makes } R_B \text{ approximately the same as } R_A \text{ at } \omega = GB.)$$

$$SR = 100nA/2pF = \underline{\underline{0.05V/\mu s}}$$

$$P_{diss} = 3V \cdot (3 \cdot 150nA) = \underline{\underline{1.35\mu W}}$$