

**Homework Assignment No. 12**Problem 1 – P7.2-1

Find the  $GB$  of a two-stage op amp using Miller compensation using a nulling resistor that has  $60^\circ$  phase margin where the second pole is  $-10 \times 10^6$  rads/sec and two higher poles both at  $-100 \times 10^6$  rads/sec. Assume that the RHP zero is used to cancel the second pole and that the load capacitance stays constant. If the input transconductance is  $500 \mu\text{A/V}$ , what is the value of  $C_c$ ?

Solution

The resulting higher-order poles are two at  $-100 \times 10^6$  radians/sec. The resulting phase margin expression is,

$$\text{PM} = 180^\circ - \tan^{-1}(A_v(0)) - 2 \tan^{-1}\left(\frac{GB}{10^7}\right) = 90^\circ - 2 \tan^{-1}\left(\frac{GB}{10^7}\right) = 60^\circ$$

$$\therefore 30^\circ = 2 \tan^{-1}\left(\frac{GB}{10^7}\right) \rightarrow \left(\frac{GB}{10^7}\right) = \tan(15^\circ) = 0.2679$$

$$GB = 2.679 \times 10^7 = \frac{g_{m1}}{C_c} \rightarrow C_c = \frac{500 \times 10^{-6}}{26.79 \times 10^7} = \underline{18.66 \text{ pF}}$$

Problem 2 – P7.2-4

Use the technique of Ex. 7.2-2 to extend the  $GB$  of the cascode op amp of Ex. 6.5-2 as much as possible that will maintain  $60^\circ$  phase margin. What is the minimum value of  $C_L$  for the maximum  $GB$ ?

Solution

Assuming all channel lengths to be  $1 \mu\text{m}$ , the total capacitance at the source of M7 is

$$C_7 = C_{gs7} + C_{bd7} + C_{gd6} + C_{bd6}$$

$$\text{or, } C_7 = 75 + 51 + 9 + 51 = 186 \text{ fF}$$

$$g_{m7} = 707 \mu\text{S}$$

Thus, the pole at the source of M7 is

$$p_{S7} = -\frac{g_{m7}}{C_7} = -605 \text{ MHz.}$$

The total capacitance at the source of M12 is

$$C_{12} = C_{gs12} + C_{bd12} + C_{gd11} + C_{bd11}$$

$$\text{or, } C_{12} = 34 + 29 + 4 + 29 = 96 \text{ fF}$$

$$g_{m12} = 707 \mu\text{S}$$

Thus, the pole at the source of M12 is

$$p_{S12} = -\frac{g_{m12}}{C_{12}} = -1170 \text{ MHz.}$$

The total capacitance at the drain of M4 is

$$C_4 = C_{gs4} + C_{gs6} + C_{bd4} + C_{gd2} + C_{bd2}$$

$$\text{or, } C_4 = 43 + 75 + 21 + 3 + 19 = 161 \text{ fF}$$

$$g_{m4} = 283 \mu\text{S}$$

Problem 2 - Continued

Thus, the pole at the drain of M4 is

$$p_{D4} = -\frac{g_{m4}}{C_4} = -280 \text{ MHz.}$$

The total capacitance at the drain of M8 is

$$C_8 = C_{gd8} + C_{bd8} + C_{gs10} + C_{gs12}$$

or,  $C_8 = 9 + 51 + 34 + 34 = 128 \text{ fF}$

$$R_2 + \frac{1}{g_{m10}} = 3.4 \text{ K}\Omega$$

Thus, the pole at the drain of M8 is

$$p_{D8} = -\frac{1}{\left(R_2 + \frac{1}{g_{m10}}\right)C_8} = -366 \text{ MHz.}$$

For a phase margin of  $60^\circ$ , we have

$$PM = 180^\circ - \left[ 90^\circ - \left\{ \tan^{-1}\left(\frac{GB}{p_{S7}}\right) + \tan^{-1}\left(\frac{GB}{p_{S12}}\right) + \tan^{-1}\left(\frac{GB}{p_{D4}}\right) + \tan^{-1}\left(\frac{GB}{p_{D8}}\right) \right\} \right]$$

Solving the above equation

$$GB \approx 65 \text{ MHz.}$$

And,  $A_v = 6925 \text{ V/V}$

Thus,  $p_1 = 9.39 \text{ KHz}$ , and  $C_L \geq 1.54 \text{ pF}$

Problem 3 - Problem 7.3-7

(a.) If all transistors in Fig. 7.3-12 have a dc current of  $50\mu\text{A}$  and a  $W/L$  of  $10\mu\text{m}/1\mu\text{m}$ , find the gain of the common mode feedback loop. (b.) If the output of this amplifier is cascoded, then repeat part (a.).

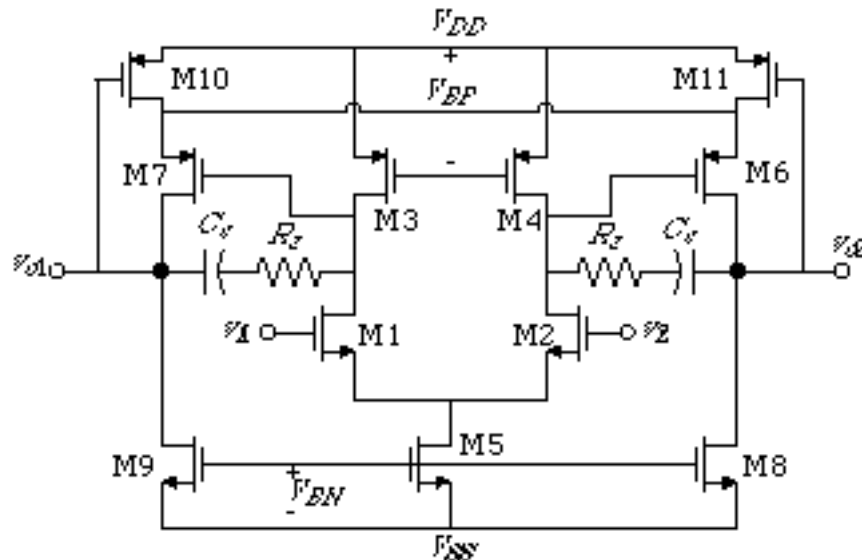
Solution

Figure 7.3-12 Two-stage, Miller, differential-in, differential-out op amp with common-mode stabilization.

Problem 3 - Continued

The loop gain of the common-mode feedback loop is,

$$\text{CMFB Loop gain} \approx -\frac{g_{m10}}{g_{ds9}} = -g_{m10}r_{ds9} \quad \text{or} \quad -\frac{g_{m11}}{g_{ds8}} = -g_{m11}r_{ds8}$$

With  $I_D = 50\mu\text{A}$  and  $W/L = 10\mu\text{m}/1\mu\text{m}$ ,  $g_{m10} = \sqrt{\frac{2K_P'W I_D}{L}} = \sqrt{2 \cdot 50 \cdot 10 \cdot 50} = 223.6\mu\text{S}$ ,

$$r_{dsN} = \frac{1}{\lambda_N I_D} = \frac{25}{50\mu\text{A}} = 0.5\text{M}\Omega \quad \text{and} \quad r_{dsP} = \frac{1}{\lambda_P I_D} = \frac{20}{50\mu\text{A}} = 0.4\text{M}\Omega$$

$$\therefore \boxed{\text{CMFB Loop gain} \approx -g_{m10}r_{ds9} = -223.6(0.5) = -111.8\text{V/V}}$$

If the output is cascoded, the gain becomes,

$$\begin{aligned} \text{CMFB Loop gain with cascoding} &\approx -\frac{g_{m10}}{g_{ds9}} g_m(\text{cascode})r_{ds}(\text{cascode}) \\ &= -g_{m10}\{[r_{ds9} g_m(\text{cascode})r_{ds}(\text{cascode})]\parallel[g_{m7}r_{ds7} (r_{ds10}\parallel r_{ds10})]\} \end{aligned}$$

$$g_{mP} = \sqrt{\frac{2K_N'W I_D}{L}} = \sqrt{2 \cdot 110 \cdot 10 \cdot 50} = 331.67\mu\text{S}$$

$$= -(223.6)[(0.5 \cdot 331.67 \cdot 0.5)\parallel(223.6)(0.4)(0.2)] = 223.6(14.7) = -3,290 \text{ V/V}$$

$$\therefore \boxed{\text{CMFB Loop gain with cascoding} \approx -3.290\text{V/V}}$$

Problem 4 – Problem 7.4-1

Calculate the gain,  $GB$ ,  $SR$  and  $P_{diss}$  for the folded cascode op amp of Fig. 6.5-7b if  $V_{DD} = -V_{SS} = 1.5\text{V}$ , the current in the differential amplifier pair is  $50\text{nA}$  each and the current in the sources, M4 and M5, is  $150\text{nA}$ . Assume the transistors are all  $10\mu\text{m}/1\mu\text{m}$ , the load capacitor is  $2\text{pF}$  and that  $n_1$  is 2.5 for NMOS and 1.5 for PMOS.

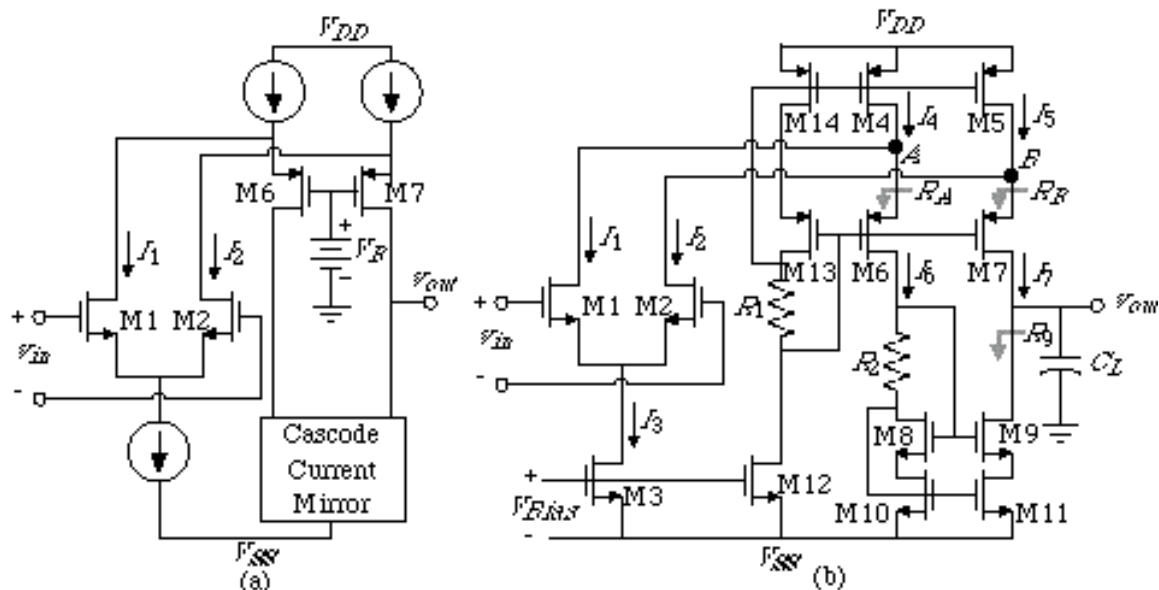


Figure 6.5-7 (a) Simplified version of an N-channel input, folded cascode op amp. (b) Practical version (a).

Problem 4 - ContinuedSolution

$$g_{m1} = g_{m2} = \frac{I_D}{n_1(kT/q)} = \frac{50\text{nA}}{2.5 \cdot 25.9\text{mV}} = 0.772\mu\text{S} \quad \text{and } r_{ds1} = r_{ds2} = \frac{1}{I_D \lambda_N} = 500\text{M}\Omega$$

$$g_{m4} = g_{m5} = \frac{I_D}{n_1(kT/q)} = \frac{150\text{nA}}{1.5 \cdot 25.9\text{mV}} = 3.861\mu\text{S} \quad \text{and } r_{ds4} = r_{ds5} = \frac{1}{I_D \lambda_N} = 133\text{M}\Omega$$

$$g_{m6} = g_{m7} = \frac{I_D}{n_1(kT/q)} = \frac{100\text{nA}}{1.5 \cdot 25.9\text{mV}} = 2.574\mu\text{S} \quad \text{and } r_{ds6} = r_{ds7} = \frac{1}{I_D \lambda_N} = 200\text{M}\Omega$$

$$g_{m8} = g_{m9} = g_{m10} = g_{m11} = \frac{I_D}{n_1(kT/q)} = \frac{100\text{nA}}{2.5 \cdot 25.9\text{mV}} = 1.544\mu\text{S}$$

$$\text{and } r_{ds8} = r_{ds9} = r_{ds10} = r_{ds11} = \frac{1}{I_D \lambda_N} = 250\text{M}\Omega$$

$$\text{Gain: } A_v(0) = g_{m1} R_{out}$$

$$R_{out} \approx r_{ds11} g_{m9} r_{ds9} \parallel [g_{m7} r_{ds7} (r_{ds5} \parallel r_{ds2})] = 96.5\text{G}\Omega \parallel 34.23\text{G}\Omega = 25.269\text{G}\Omega$$

$$\therefore A_v(0) = 0.772\mu\text{S} \cdot 25.269\text{G}\Omega = \underline{19,508 \text{ V/V}}$$

$$GB = g_{m1}/C_L = 386\text{krads/sec} = \underline{61.43\text{kHz}} \quad (\text{this assumes all other poles are greater than}$$

$GB$  which is the case if  $C_L$  makes  $R_B$  approximately the same as  $R_A$  at  $\omega = GB$ .)

$$SR = 100\text{nA}/2\text{pF} = \underline{0.05\text{V}/\mu\text{s}} \quad P_{diss} = 3\text{V} \cdot (3 \cdot 150\text{nA}) = \underline{1.35\mu\text{W}}$$

Problem 5 – Pre-charge Buffer Design Problem

(Solution not available)